



Ollscoil  
Teicneolaíochta  
an Atlantaigh

Atlantic  
Technological  
University

BEng(H) Software & Electronic Engineering

System on Chip Design & Verification  
Year 3

FPGA Stopwatch Project Assignment

**Dan Koskiranta**

Atlantic Technological University Galway  
2023 - 2024

## Table of Contents

1. Introduction .....	3
2. Project Setup and Configuration .....	4
3. Simulation .....	5
4. RTL Analysis .....	7
5. Synthesis & Implementation .....	12
6. Basys3 FPGA Development Board Demonstration.....	13
7. Code Analysis.....	14
8. Design Adaptation .....	15
9. Problem Solving .....	16
10. References .....	17

## **1. Introduction**

The purpose of this project is to create a digital stopwatch on a reconfigurable System-on-Chip (SoC) platform. The digital stopwatch is created by integrating the hardware description FPGA technology and the Xilinx Vivado toolchain. The stopwatch will initially display three digits on the Basys3 FPGA Development Board. At the end of the project, code is modified to display four digits.

The project involves the testing and simulation of Verilog code to make sure the code works as expected. This is followed by synthesis to transform the code into a netlist to represent the logical structure of the design. Final part is the implementation to map the netlist on the target FPGA architecture and generate bitstream to configure the FPGA with the desired functionality.

## 2. Project Setup and Configuration

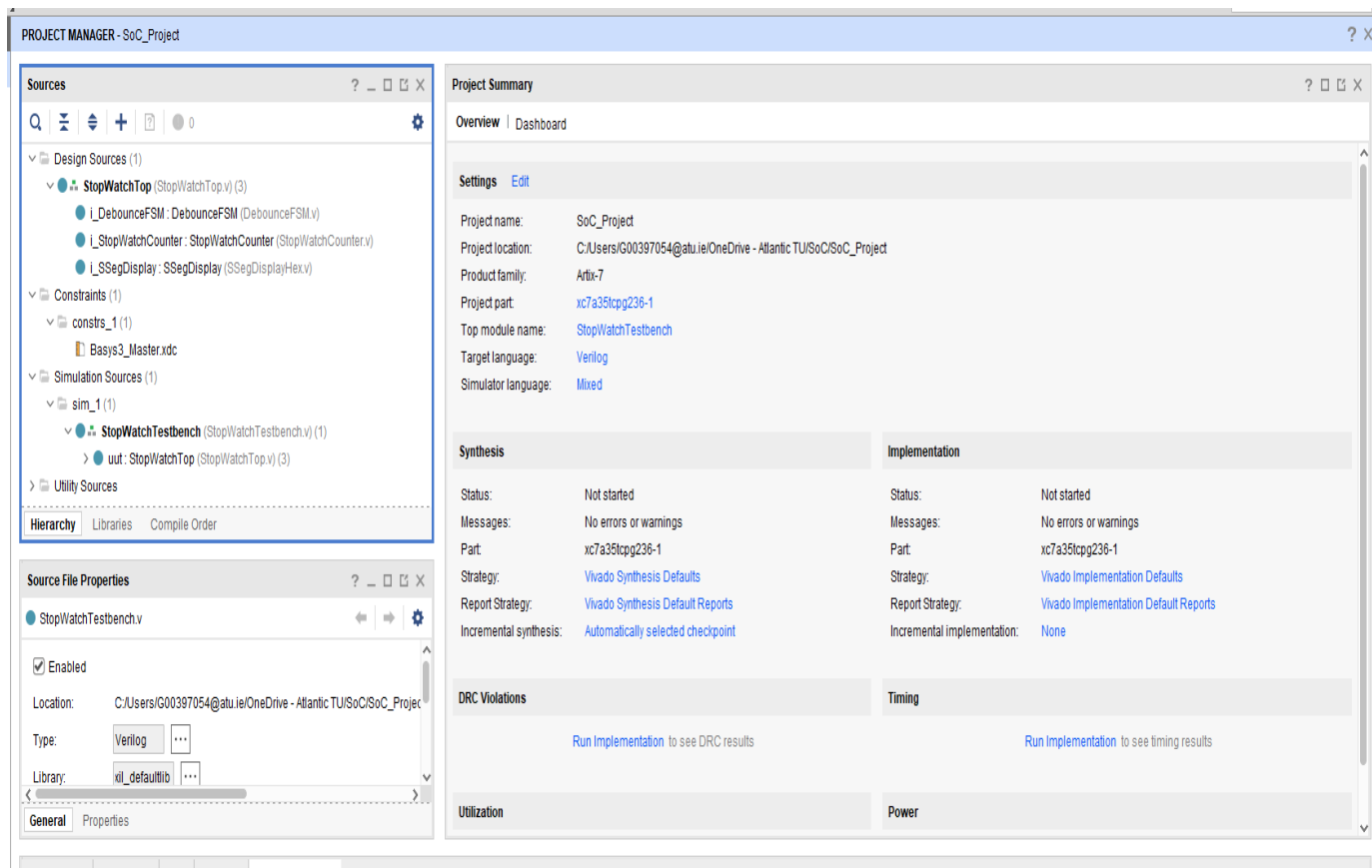


Figure 1 Vivado Project Window

Figure 1 shows the Sources Panel with project hierarchy.

### 3. Simulation

It's very important to test your design to make sure your hardware works as expected. Untested design and dysfunctional hardware might lead to big financial losses.

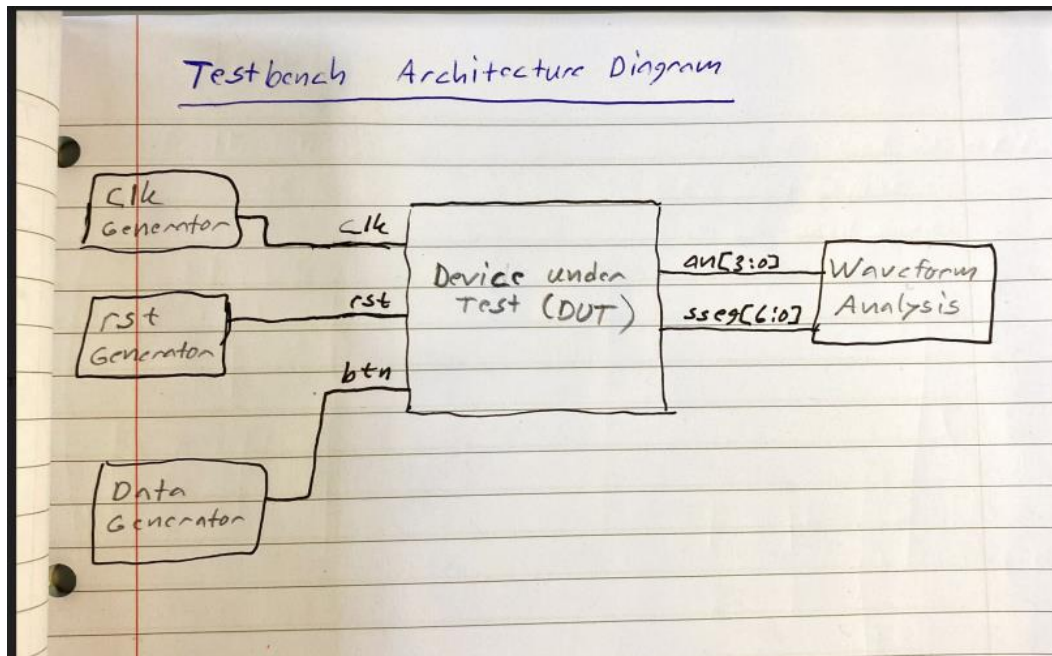


Figure 2 Testbench Architecture Diagram

Testbench is the simulation environment used to verify the functionality of your digital design before synthesizing it and implementing it on hardware.

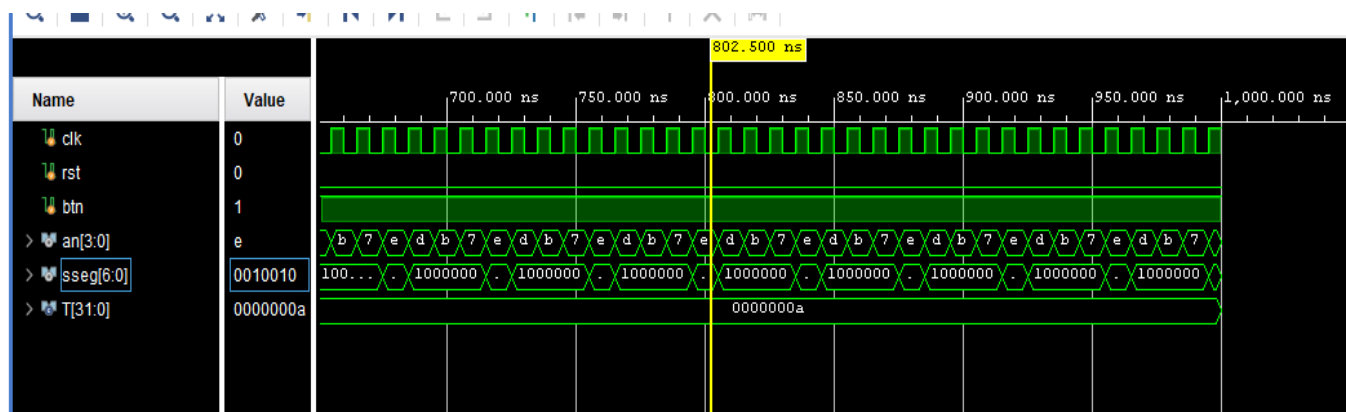



Figure 3 Simulation Waveform

The clock clk input makes the output change each time the clock input goes from LOW to HIGH. The reset rst returns the counter to zero.

The btn signal generates the data. The 7-segment display won't start counting before btn goes HIGH.

an[3:0] represents the internal signals. There are 4 bits on the an signal and the an signal drives the 7-segment display.

The line sseg[6:0] represents the 7-segment displays. Number 1 on the 7-bit value indicates which segment (LED) is off on the 7-segment display.

 

**Figure 4: 7-segment Display**

g f e d c b a

0 = 1 0 0 0 0 0 0

**Figure 4** represents a seven-segment display.

#### 4. RTL Analysis

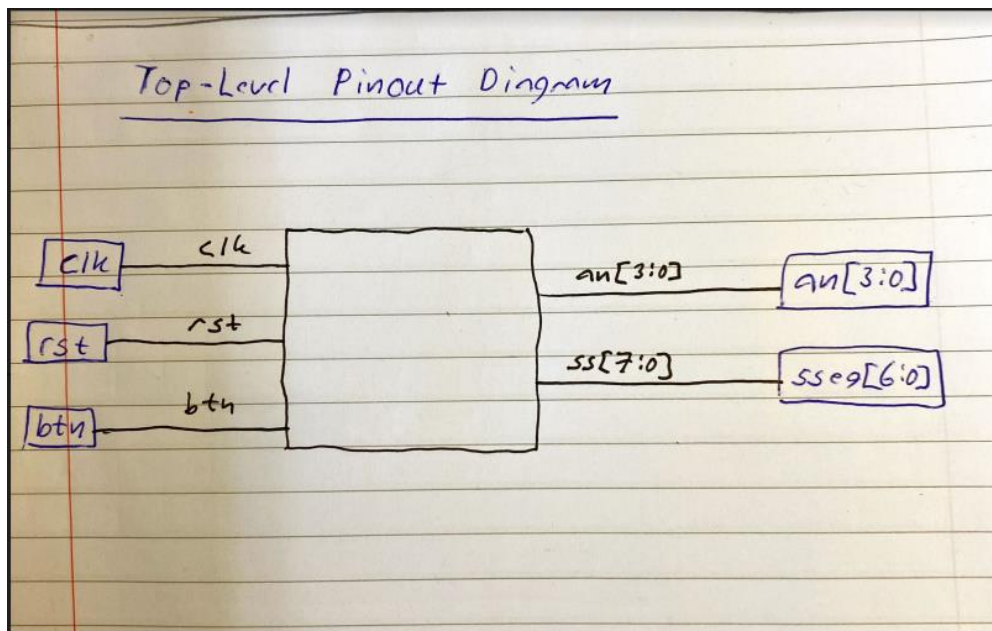


Figure 5 Top-Level Pinout Diagram for StopWatch Module

The StopWatch top module in **figure 5** contains all the other modules. It coordinates the operation of a stopwatch. The functionality is to create a stopwatch system that can be started, stopped, and reset.


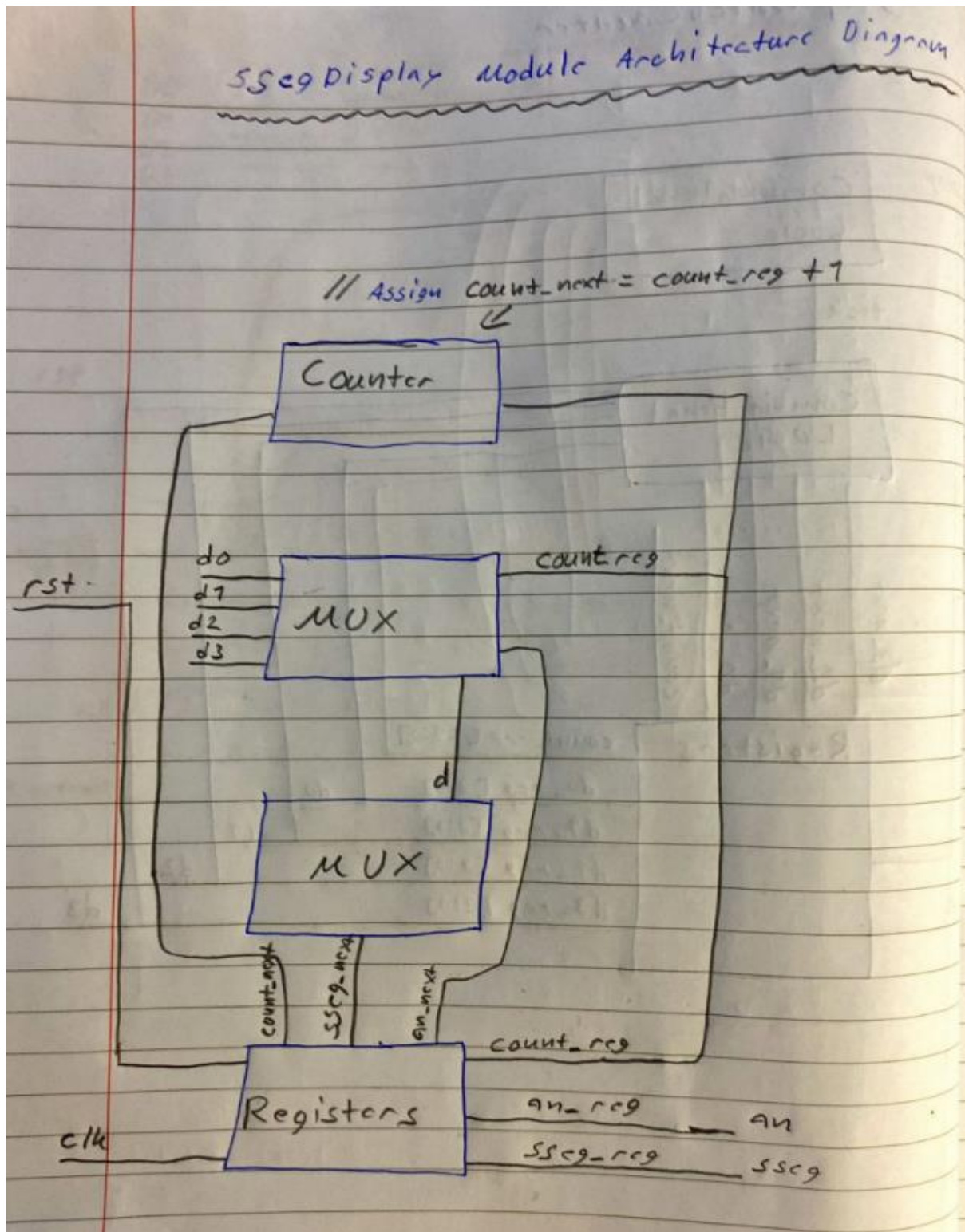


Figure 6 SSegDisplay Module Architecture Diagram

The SSegDisplay Module in **figure 6** is designed for multiplexing a seven-segment display, which displays numbers between 0 and 9 and hexadecimal numbers A to F.

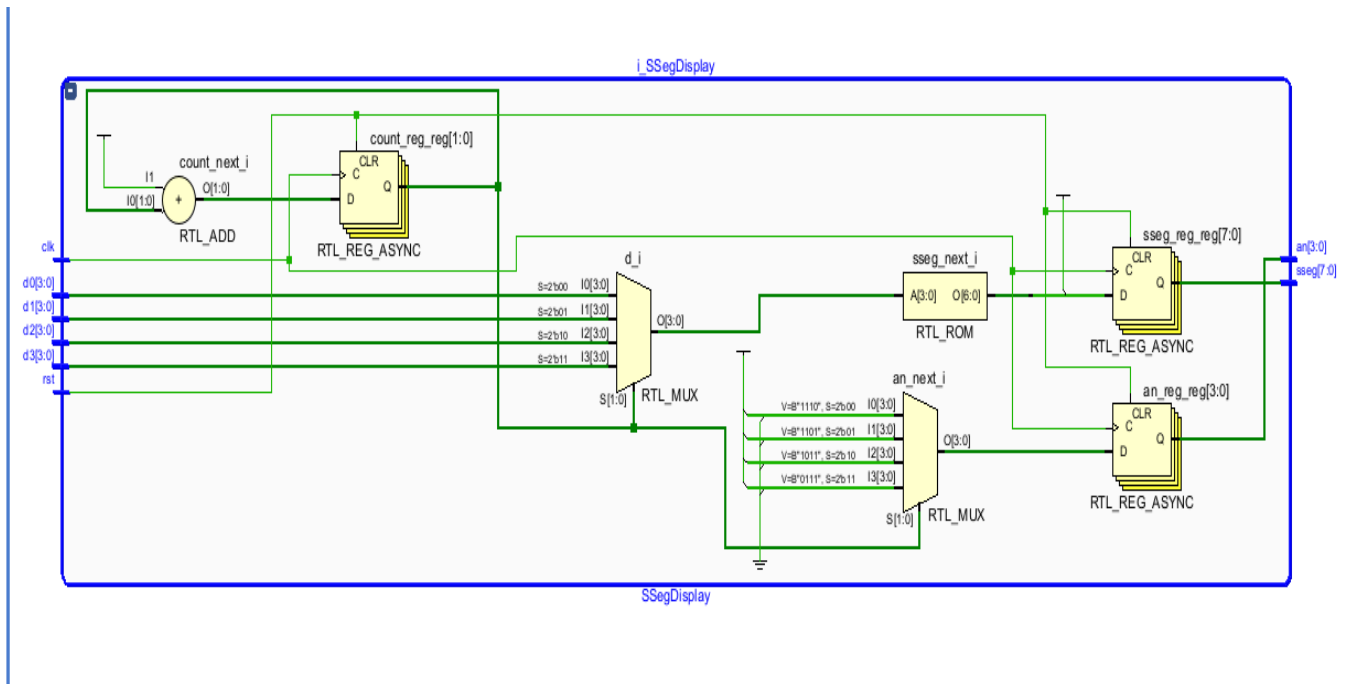



**Figure 2 Elaborated Design Schematic for SSegDisplay Module**

FPGA hardware elements used to implement the Verilog code. Match each hardware element to a piece of the Verilog code for this module:

Code: input wire [3:0] d3, d2, d1, d0, is associated with RTL\_MUX

count\_reg = counter register.

an\_reg = 4 bit register for controlling the common anode.

sseg\_reg = 8-bit register for driving the segments.

count\_next = wire used to calculate the next value of the counter.

sseg\_next = wire to represent the next value for driving the segments of a 7-segment display. Code below is for sseg\_next:

4'h0: sseg\_next[6:0] = 7'b1000000; // all leds on, bar g, for digit 0

4'h1: sseg\_next[6:0] = 7'b1111001; // leds b, c on for digit 1

4'h2: sseg\_next[6:0] = 7'b0100100; // leds c, f off for digit 2

4'h3: sseg\_next[6:0] = 7'b0110000; // leds e, f off for digit 3

```

4'h4: sseg_next[6:0] = 7'b0011001;
4'h5: sseg_next[6:0] = 7'b0010010;
4'h6: sseg_next[6:0] = 7'b0000010;
4'h7: sseg_next[6:0] = 7'b1111000;
4'h8: sseg_next[6:0] = 7'b0000000; // all leds on for digit 8
4'h9: sseg_next[6:0] = 7'b0010000;
4'ha: sseg_next[6:0] = 7'b0001000;
4'hb: sseg_next[6:0] = 7'b0000011;
4'hc: sseg_next[6:0] = 7'b1000110;
4'hd: sseg_next[6:0] = 7'b0100001;
4'he: sseg_next[6:0] = 7'b0000110;
4'hf: sseg_next[6:0] = 7'b0001110; // leds b, c, d off for hex digit F
default: sseg_next[6:0] = 7'b1111111; // all off

```

---

**an\_next** = 4-bit wire for representing the next value for controlling the common anode of a 4-digit 7-segment display.

**d** = 4-bit wire used to multiplex the digit input.

Code below is representing the **an\_next** and **d**:

```

always @* begin
  case(count_reg[N-1:N-2])
    2'b00: begin // Rightmost digit display on
      an_next = 4'b1110;
      d      = d0;
    end
    2'b01: begin // Second display from right on
      an_next = 4'b1101;
      d      = d1;
    end
  end

```

```
2'b10: begin // Third display from right on
    an_next = 4'b1011;
    d      = d2;
end
2'b11: begin // Leftmost display on
    an_next = 4'b0111;
    d      = d3;
end
default: begin // Default, no display on
    an_next = 4'b1111;
    d      = 4'b0000;
end
endcase
end
```

## 5. Synthesis & Implementation

- 1: Bigger NUM\_CLK\_CYCLES value allows the synthesis tool to gather more accurate timing information about the design. Smaller value in simulation helps with faster verification and debugging.
- 2: 10,000,000 with a 100MHz clock sets d0 tick at 0.1s  
Calculate the value of NUM\_CLK\_CYCLES required so that the rightmost digit, d0, will count in hundredths of seconds.  
$$\text{NUM\_CLK\_CYCLES} = 0.01 \text{ s} \times (100 \times 10^6)$$
$$\text{NUM\_CLK\_CYCLES} = 1000\ 000$$
- 3: After the code has been tested, next part is synthesis and implementation. The synthesis converts the code into a netlist which is a list of components that fit the target circuit. Next, the implementation tool will take the netlist as input and does the placing and routing for the design. Implementation is where the physical locations of the logic elements are determined. Finally, a bitstream is generated for programming the FPGA.
4. Resource utilization is crucial for optimizing a design to meet performance and resource Constraints. Resource utilization provides insights into the logical-to-physical mapping of the design. This will help to optimize the code for a specific FPGA design.

## 6. Basys3 FPGA Development Board Demonstration

 


Figure 8: Stopwatch working on the Basys3 FPGA Development Board.

## 7. Code Analysis

Code for the StopWatchCounter module uses the ternary operator in assigning values to two signals: count\_next and tick. Re-write this code in both cases, as pseudo-code, to use if-else statements instead of the ternary operator.

```
assign count_next = (rst || (count_reg == NUM_CLK_CYCLES && go)) ? 4'b0 : (go) ?  
count_reg + 1 : count_reg;  
assign tick = (count_reg == NUM_CLK_CYCLES) ? 1'b1 : 1'b0;
```

---

### Rewritten code using if-else statements (Pseudo code)

```
if(rst || (count_reg == NUM_CLK_CYCLES && go))  
    count_next = 4'b0;  
else if(go)  
    count_next + 1;  
else  
    count_next = count_reg;
```

---

```
if(count_reg == NUM_CLK_CYCLES)  
    tick = 1'b1;  
else  
    tick = 1'b0;
```

## 8. Design Adaptation

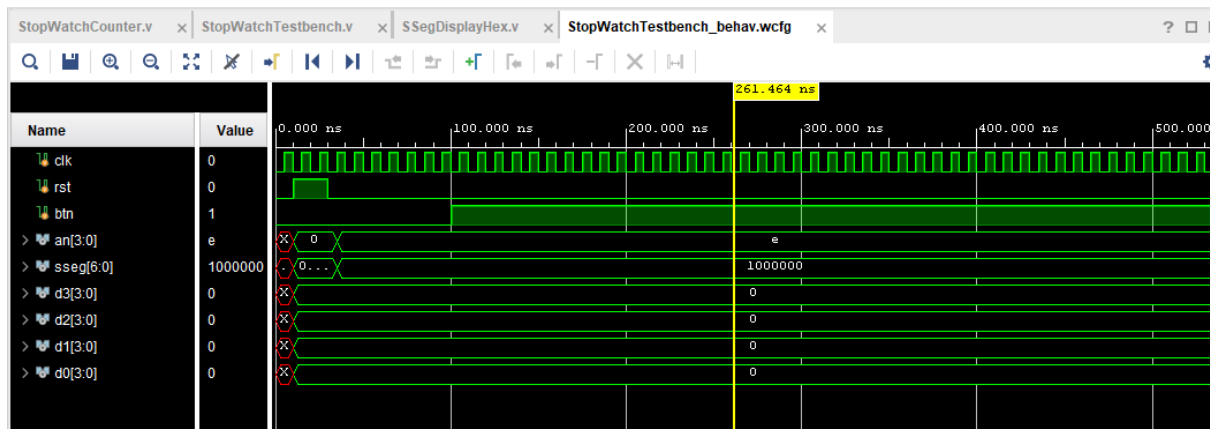


Figure 9: Simulation output of the enhanced design implementing the four digits in Vivado.

 


Figure 10: Enhanced design to implement 4 digits on the Basys3 FPGA Development Board.

## 9. Problem Solving

```
if (tick) begin
    if (d0_reg != 9) begin           // d0 has not yet reached 9, keep incrementing
        d0_next = d0_reg + 1;
    end
    else begin                       // d0 is 9, number is xxx9
        d0_next = 4'b0000;          // reset d0
        if(d1_reg != 9) begin       // now check d1, increment if not yet 9
            d1_next = d1_reg + 1;
        end
        else begin                  // d1 is 9, number is xx99
            d1_next = 4'b0000;      // reset d1
            if(d2_reg != 9) begin    // now check d2, increment if not yet 9
                d2_next = d2_reg + 1;
            end
            else begin              // d2 is 9, number is x999
                d2_next = 4'b0000;   // reset d2
                if(d3_reg != 9) begin
                    d3_next = d3_reg + 1;
                end
                else begin
                    d3_next = 4'b0000;
                    if(d4_reg != 9) begin
                        d4_next = d4_reg + 1;
                    end
                    else begin
                        d4_next = 4'b0000;
                    end
                end
            end
        end
    end
end // end if(tick)
end // end else if(rst)
end
```

Figure 11: Problem Solving Example

The biggest problem I encountered during this project was the implementation of the fourth digit on the Basys3 FPGA Development Board. Initially, I was trying to run the code with the four outputs:

```
assign d0 = d0_reg;
assign d1 = d1_reg;
assign d2 = d2_reg;
assign d3 = d3_reg;
```

However, I was unable to get this work. So, I added a fifth output: `assign d4 = d4_reg`. After this, I ran into problems with synthesizing it. It turned out that I was missing an **end** keyword in the code block that increments the four-digit counter.



## 10. References

- [1] Digilent, "Basys 3 Reference," 2021. [Online]. Available: <https://reference.digilentinc.com/basys3/refmanual>.
- [2] P. J. Ashenden, Digital Design (Verilog): An Embedded Systems Approach Using Verilog, Burlington: Morgan Kaufmann, 2007.
- [3] M. Lynch, "Combinational and Sequential Logic with Verilog & Xilinx Vivado," 2021. [Online]. Available: <https://learnonline.gmit.ie>.
- [4] M. Lynch, "FPGA Stopwatch Project Source Code," 2021. [Online]. Available: <https://learnonline.gmit.ie>.
- [5] "chat.openai.com," OpenAI, 30 11 2022. [Online]. Available: <https://chat.openai.com/chat>. [Accessed 5 12 2023].